



Sri Chaitanya IIT Academy, India

A.P, TELANGANA, KARNATAKA, TAMILNADU, MAHARASHTRA, DELHI, RANCHI

A right Choice for the Real Aspirant

ICON CENTRAL OFFICE, MADHAPUR-HYD

Sec: Sr. IPLCO

JEE ADVANCED

DATE : 08-11-15

TIME : 02:00 AM TO 05:00 PM

2013_P2 MODEL

MAX MARKS : 180

KEY & SOLUTIONS

PHYSICS

1	B	2	AB	3	BCD	4	ABC	5	ABC
6	ABD	7	ACD	8	BCD	9	B	10	A
11	B	12	B	13	C	14	B	15	A
16	D	17	D	18	B	19	C	20	A

CHEMISTRY

21	ABC	22	BCD	23	ABCD	24	BCD	25	ABCD
26	ABC	27	ABCD	28	ABCD	29	B	30	C
31	C	32	C	33	C	34	B	35	A
36	C	37	C	38	A	39	D	40	B

MATHEMATICS

41	AC	42	ABC	43	ABD	44	BC	45	ABD
46	ABCD	47	ABCD	48	ABD	49	C	50	B
51	B	52	C	53	A	54	B	55	A
56	D	57	D	58	A	59	D	60	C

PHYSICS

1. [Sol. (B)]

Method I

Force between plates

$$F = \frac{Q^2}{2n\epsilon_0} = \frac{\left(\frac{\epsilon_0 A V}{x}\right)^2}{2 A \epsilon_0} = \frac{\epsilon_0 A V^2}{2 x^2} \text{ where } x \text{ is separation between plates}$$

$$dW = F dx$$

$$W = \int_d^{2d} \frac{\epsilon_0 A V^2}{2 x^2} dx = \frac{\epsilon_0 A V^2}{4 x} = \frac{C V^2}{4} = 200 \mu J$$

Method II

$$U_{\lambda} + W_B + W_{\text{ext}} = U_f + \text{loss}$$

Process is slow so energy loss is zero work done by battery = $W_B = QE$

$$Q = Q_f - Q_i = 20 - 40 = -20$$

$$W_B = -20 \times 20$$

$$2 \times 20^2 - 20 \times 20 + W_{\text{ext}} = 1 \times 20^2 + 0$$

$$W_{\text{ext}} = 200 \mu J$$

2. [Sol. (A,B)]

Potential difference across 'C₁'

$$V_1 = \frac{C_2 V}{C_1 + C_2} = \frac{V}{1 + C_1/C_2}$$

When dielectric is inserted C₂ will increase.

3. [Sol. (B,C,D)]

Rate of change of energy = V.I.


Initially V = 0 hence VI = 0

finally I = 0 hence VI = 0

∴ first increases then decreases

4. [Sol. (A,B,C)]

$$V = \frac{Q_1 + Q_2}{C_1 + C_2} = 0$$

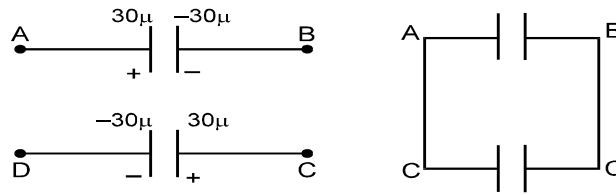

Final potential difference = zero


Final charge = Zero

Charge flow $30 \mu\text{C}$ A to D from A to D

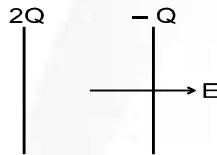5. [Sol. (A,B,C)]

$$E = \frac{2Q}{2A\epsilon_0} + \frac{Q}{2A\epsilon_0} \Rightarrow E = \frac{3Q}{2A\epsilon_0}$$

$$E = \frac{3Q}{2Cd} \Rightarrow Ed = \frac{3Q}{2C} = V$$



(ii) $F = EQ$

$$F = \left(\frac{2Q}{2A\epsilon_0} \right) \times (-Q) = -\frac{Q^2}{A\epsilon_0}$$

$$F = \frac{Q^2}{A\epsilon_0}$$

$$(iii) \text{ Energy} = \frac{1}{2} \epsilon_0 E^2 Ad = \frac{1}{2} \epsilon_0 \left(\frac{3Q}{2Cd} \right)^2 Ad = \frac{9Q^2}{8C}$$

6. [Sol. (A,B,D)]

As voltage applied across capacitor is same i.e. 10V in both case.

Therefore in both case

$$Ed = 10 \Rightarrow E = \frac{10}{d}, \text{ as } d \text{ is constant. Therefore electric field remains the}$$

same as 10 V/m

7. [Sol. (A,C,D)]

8. [Sol. (B,C,D)]

Capacitor is directly connected with 1 V cell in parallel to it

$$\therefore Q = CV = 1 \times 1 = 1 \mu\text{C}$$

9. [Sol. (B)]

$$\frac{1}{\rho} = \frac{Ne^2\tau}{m}$$

$$\text{hence } \tau = \frac{m}{\rho Ne^2} = \frac{9.1 \times 10^{-31}}{(1.6 \times 10^{-8} \times 8 \times 10^{28} \times 1.6 \times 10^{-19} \times 1.6 \times 10^{-19})} \approx 2.77 \times 10^{-14} \text{ sec.}$$

10. [Sol (A)]

$$S = 2 \times 10^{-4} \times 10 = 2 \times 10^{-3}$$

$$E = \rho J = 1.6 \times 10^{-8} \times \frac{2.56}{10^{-6}}$$

$$v = Es = 80 \mu\text{V}]$$

11,12 [Sol. (b,b) At $E_2 = 4$ No current from E_2 & 0.1 A from E_1

$$E_1 - 0.1(R_1 + R_2) = 0 \quad \dots(1)$$

$$E_1 - 0.1R_1 = 4 \quad \dots(2)$$

$$\text{At } E_2 = 6 \text{ No current from } E_1 \Rightarrow E_1 = 6 \text{ V}$$

$$\therefore R_1 = 20 \Omega$$

$$\& \quad 6 = 0.1(20 + R_2) \Rightarrow R_2 = 40 \Omega]$$

13. [Sol. (C)]

14. [Sol. (B)]

15. [Sol. (A) Electric field will be from A to B]

16. [Sol. (D) Electric field can be either from A to B or from B to A depending on which is plate is positively charged.]

17. [Sol. (D)]

18. [Sol. (B)]

19. [Sol. (C)]

20. [Sol. (A)]